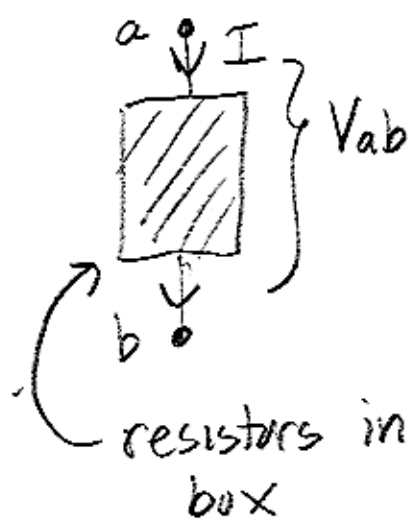


Chapter 27 - DC Circuits

- 1) Resistors in series + parallel
- 2) Kirchoff's Rules
- 3) Meters
- 4) RC Circuits
- 5) Power Distribution


Series + Parallel Resistors



$$V_{ab} = I R_{eq}$$

defines R_{eq}

For
Example

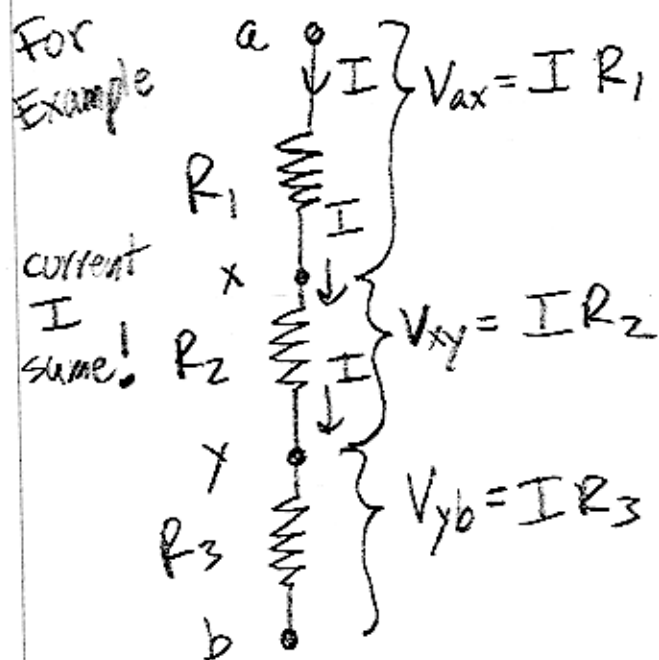

$$V_{ab} = V_{ax} + V_{xy} + V_{yb}$$


$$= IR_1 + IR_2 + IR_3$$

$$V_{ab} = I(R_1 + R_2 + R_3)$$

$$R_{eq} = R_1 + R_2 + R_3$$

resistors in
series

(more resistors, keep adding)

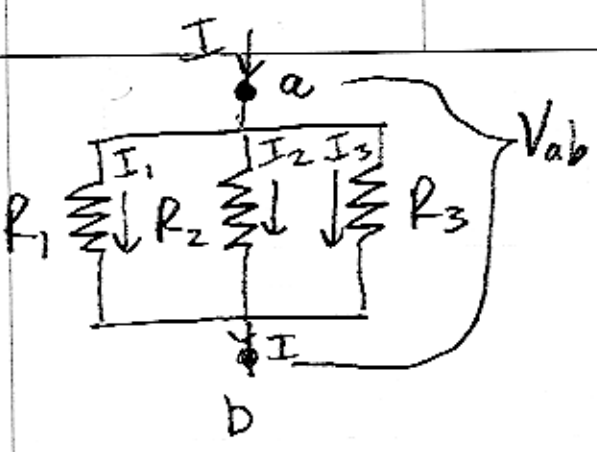

$$V_{ab} = I_1 R_1 = I_2 R_2 = I_3 R_3$$

$$I = I_1 + I_2 + I_3$$

$$\uparrow \quad \quad \uparrow \quad \quad \uparrow$$

$$\frac{V_{ab}}{R_1} \quad \frac{V_{ab}}{R_2} \quad \frac{V_{ab}}{R_3}$$

$$I = V_{ab} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$R_{eq} I = V_{ab}$$

$$I = V_{ab} \cdot \frac{1}{R_{eq}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$1/R_{eq}$ is larger than any of $1/R_1, 1/R_2, 1/R_3$

so, R_{eq} is smaller than any of R_1, R_2, R_3


note: $V_{ab} = I_i R_i$

$$I_i = \frac{V_{ab}}{R_i} \Rightarrow I \propto \frac{1}{R}$$

parallel: most current flows through smallest resistor.

series: most voltage across largest resistor

Two parallel resistors

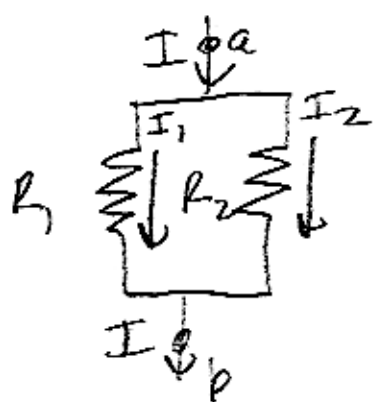

$$V_{ab} = R_{eq} I$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\frac{1}{R_{eq}} = \frac{R_2 + R_1}{R_1 R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

when $R_1 \ll R_2 \Rightarrow \frac{R_1 R_2}{R_2} = R_1$

$R_2 \ll R_1 \Rightarrow \frac{R_1 R_2}{R_1} = R_2$


"small one dominates"

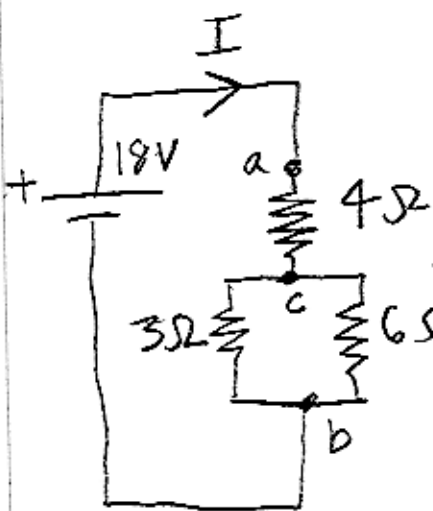


- Find I ... everywhere
- simplify resistors

$$\frac{1}{R} = \frac{1}{3\Omega} + \frac{1}{6\Omega} = \frac{3}{6} \frac{1}{\Omega}$$


$$R = 2\Omega$$

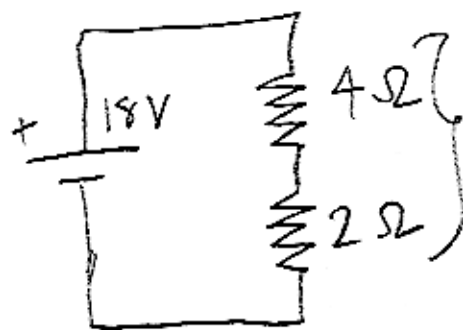

$$R' = 4 + 2 \Rightarrow -6\Omega$$

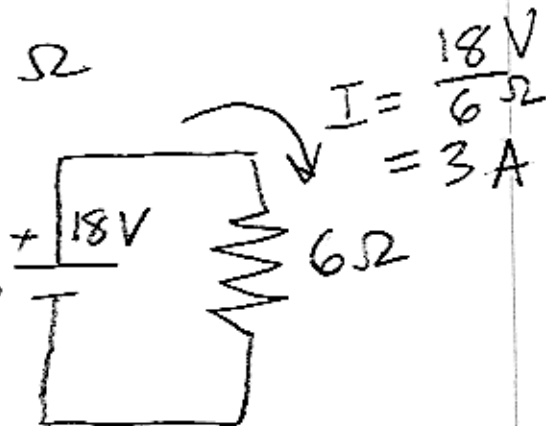


Now "unwind"

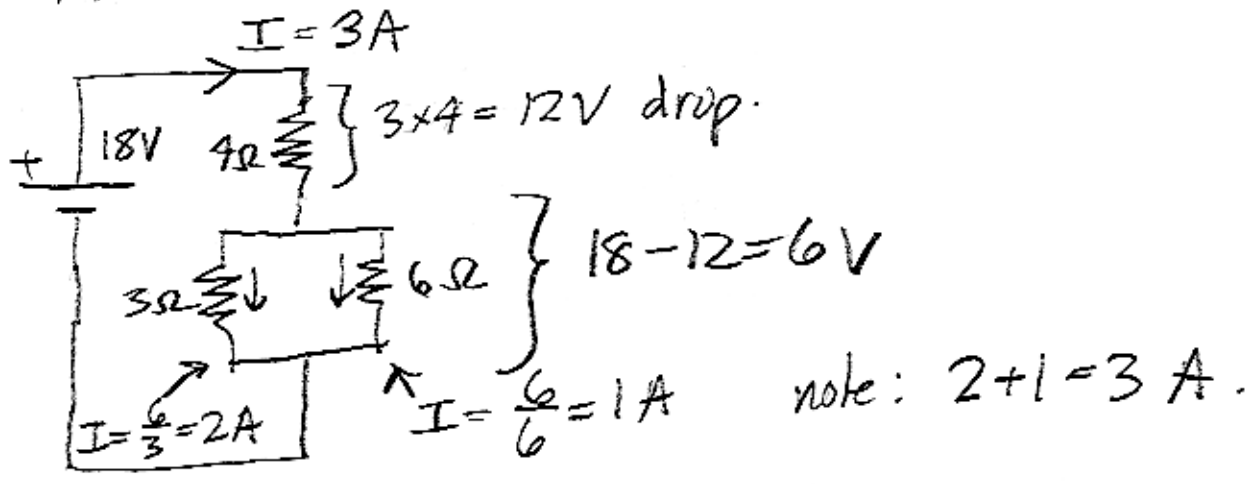

Kirchoff's Rules

... tell you what to do for complex circuits.

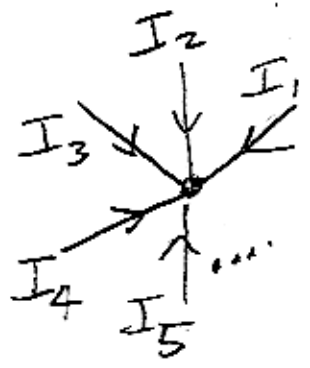① at a junction of wires, all incoming current must be carried out ... mathematically



$$I_1 + I_2 + I_3 + I_4 + I_5 + \dots$$

$$\text{or } \sum I_i = 0 = \bigcirc$$

simple case:



$$I_1 + I_2 = 0$$

$$I_2 = -I_1$$


- sign means, reverse direction

means:



(charge never accumulates or disappears)

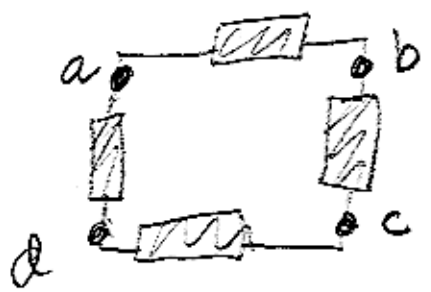
② Around a loop of circuit elements, there is no net voltage...



$$V_{ab} + V_{bc} + V_{cd} + V_{da} = 0$$

$$\sum_i V_i = 0$$

Example: Battery Charging

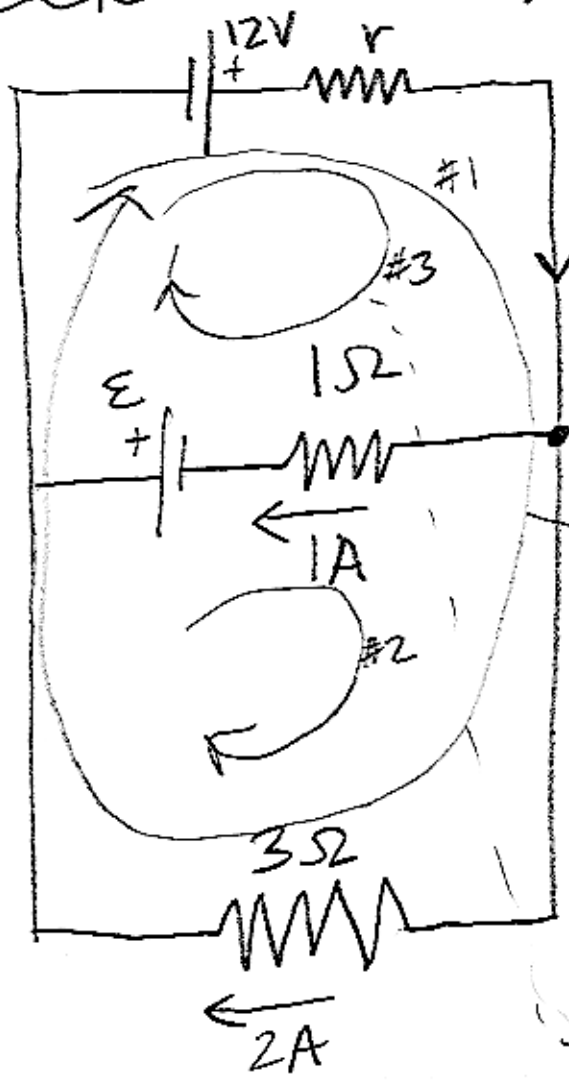

Find \mathcal{E}
and r
→ 2 unknowns
→ 2 loops

$$I = 1 + 2 = 3A$$

this loop, #1

$$-I \cdot r - 2 \cdot 3 + 12 = 0$$

drop
drop
rise

$$-3 \cdot r + 6 = 0$$

$$r = 6/3 = 2\Omega$$

this loop, #3

$$-I r - 1 \cdot 1 + \mathcal{E} + 12 = 0$$

$$-6 - 1 + \mathcal{E} + 12 = 0$$

$$\mathcal{E} = -5V$$




Cross check:
#2

$$-E + 1.1 - 3.2 = 0$$


$$+5 + 6 - 6 = 0$$

$$0 = 0$$

Important:

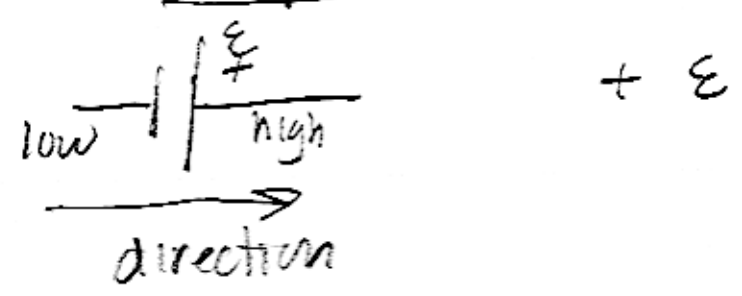


$$+ \mathcal{E}$$

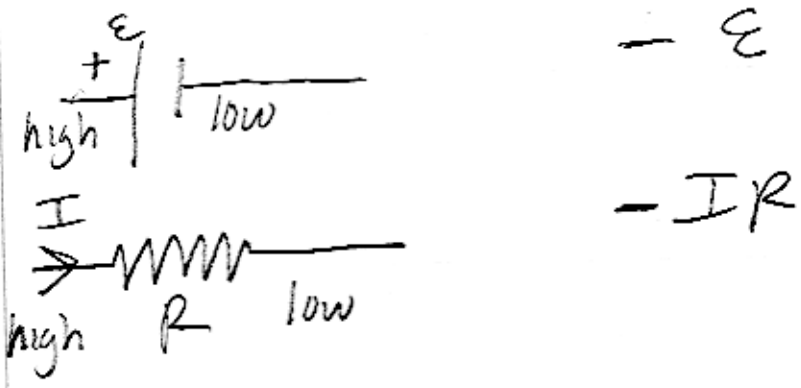



$$- \mathcal{E}$$

$$- IR$$

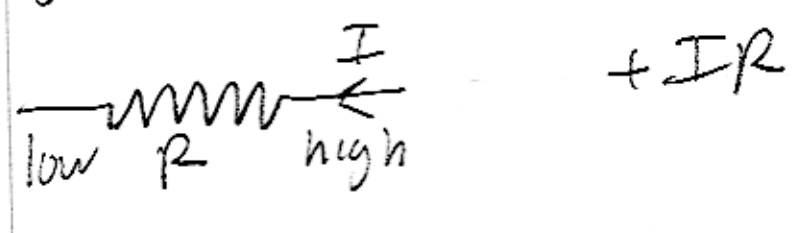

$$+ IR$$

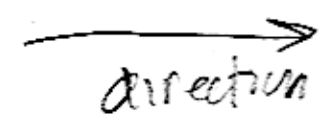

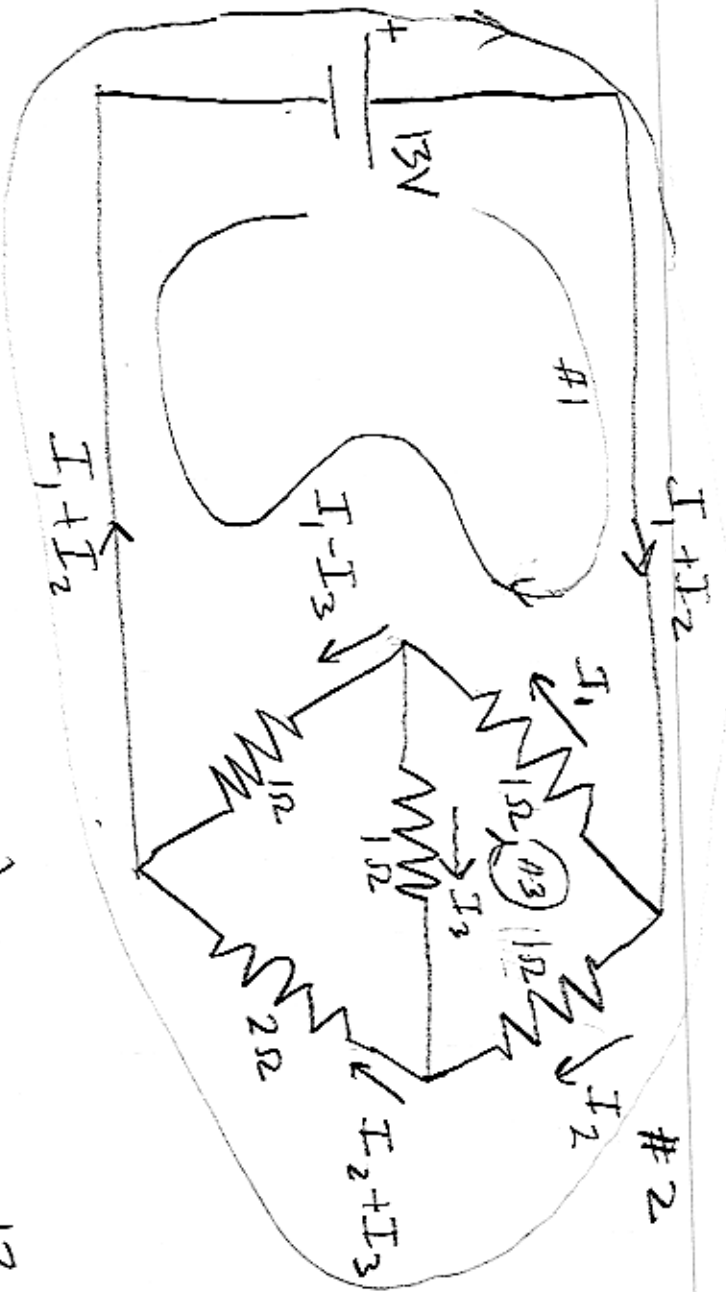

3 unknowns
need 3
equations

100pts; #1: $13V - I_1 \cdot 1 - (I_1 - I_3) \cdot 1 = 0 \Rightarrow 13 - 2I_1 + I_3 = 0$

#2: $13V - I_2 \cdot 1 - (I_2 + I_3) \cdot 2 = 0 \Rightarrow 13 - 3I_2 - 2I_3 = 0$

#3: $I_1 \cdot 1 - I_2 \cdot 1 + I_3 \cdot 1 = 0 \Rightarrow I_1 - I_2 + I_3 = 0$
 $I_2 = I_1 + I_3$

#1: $13 = 2I_1 - I_3 = 2I_1 - I_3$

#2 + #3 $\Rightarrow 13 = 3 \cdot (I_1 + I_3) + 2I_3 = 3I_1 + 5I_3$

$$\#1 \times 5: \quad 65 = 10I_1 - 5I_3$$

$$\#2': \quad 13 = 3I_1 + 5I_3$$

$$78 = 13I_1$$

$$I_1 = 6A$$

sub into #2:


$$13 = 3 \cdot 6 + 5 \cdot I_3$$

$$13 - 18 = -5 = 5I_3$$

$$I_3 = -1A$$

$$I_2 = I_1 + I_3 = 6 - 1 = 5A$$

$$I_1 + I_2 = 6 + 5 = 11A$$

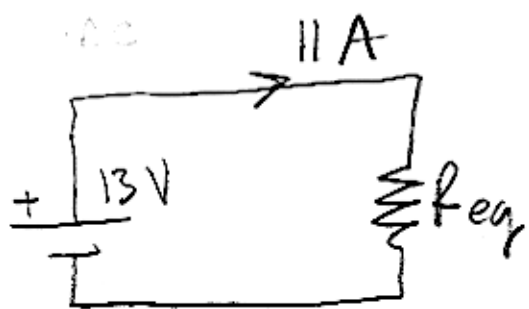

$$R_{eq} \cdot 11A = 13V$$

$$R_{eq} = \frac{13}{11} = 1.2 \Omega$$