
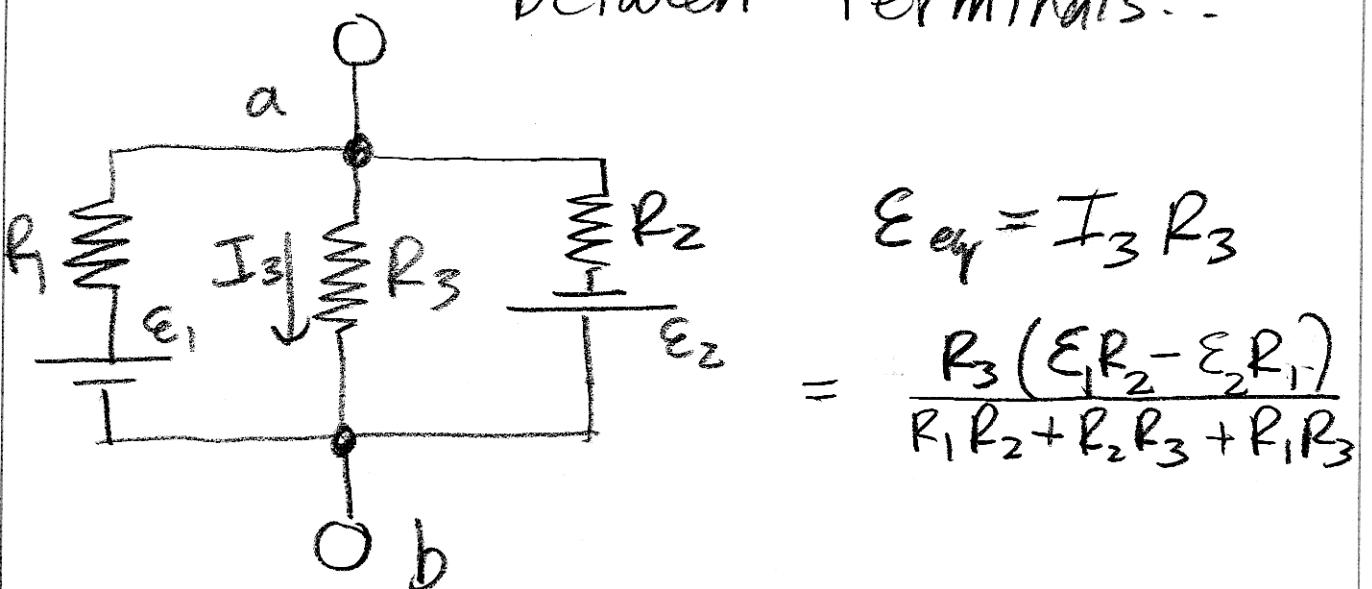


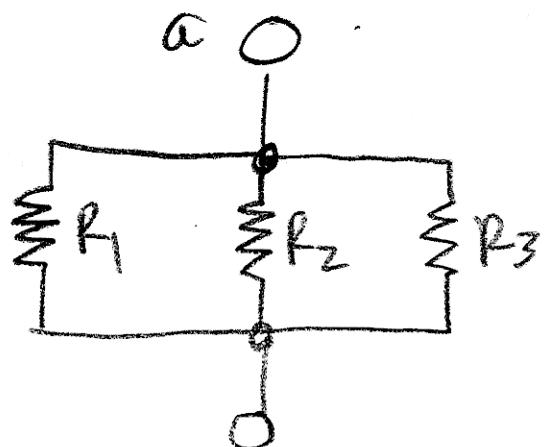①  $E_{eq}$  = voltage you get between external terminals when nothing connected between terminals.




②  $R_{eq}$  = Resistance between terminals when  $E_1 = E_2 = 0$




$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{eq} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

Proof?  $\rightarrow$  linearity

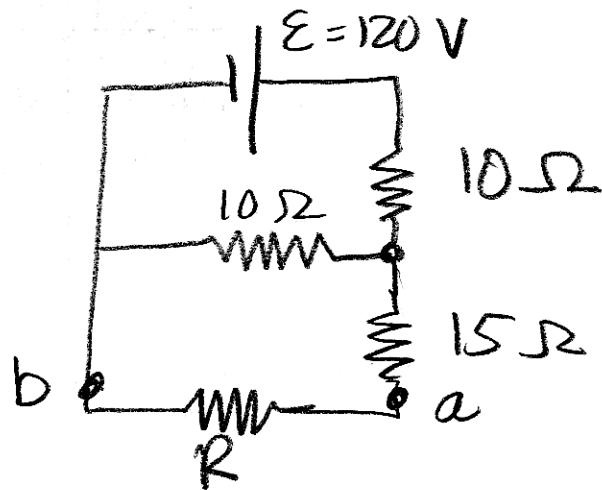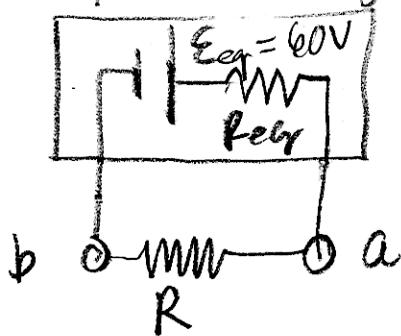
Problem 4.22:

What value of  $R$  maximizes the power dissipated in  $R$ ? Thévenin:  $R = \infty$ ,  
only 2  $10\Omega$  to ground:  $E_{eq} = \frac{1}{2} \cdot 120V = 60V$




$$E_{eq} = 60V$$

$$R_{eq} \Rightarrow$$

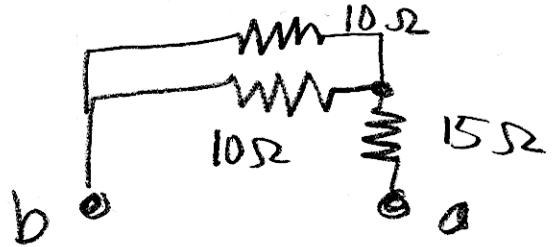

$$I = \frac{E_{eq}}{(R + R_{eq})}$$

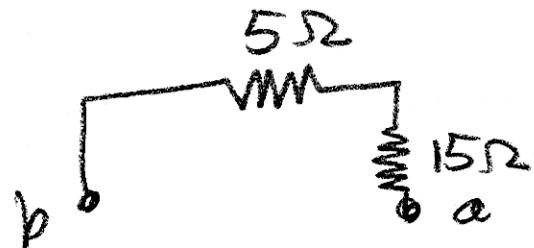

$$R_{eq} = 20\Omega$$

$$P = I^2 R = \frac{R}{(R + R_{eq})^2} \cdot E_{eq}^2$$

in video,  
neglected  
one power  
of  $E_{eq}$

$$\frac{dP}{dR} = \frac{1}{(R + R_{eq})^2} = \frac{2R}{(R + R_{eq})^3} = \frac{R_{eq} + R - 2R}{(R + R_{eq})^3} = 0$$


Then  $R = R_{eq} = 20\Omega$

$$P = \frac{20}{40} \cdot \frac{1}{40} \cdot 60^2$$

$$P = \frac{3}{4} \cdot 60 = 45W$$
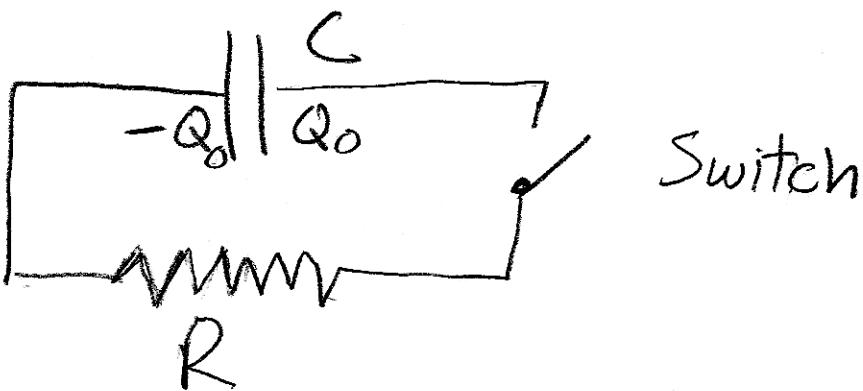
## RC Circuits


A case where "steady state" is not the case.



$-\infty < + < 0$ : switch open

$Q_0, -Q_0$  on capacitor ...  $V_0 = \frac{Q_0}{C}$   
across capacitor.

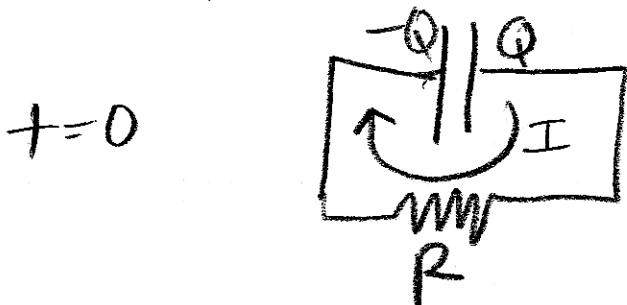$+ = 0$ : Switch closes! Current starts to flow across resistor



$$I(0) = \frac{V_0}{R} = \frac{Q_0}{RC}$$

$+ \rightarrow \infty$  ...  $I \rightarrow 0, Q \rightarrow 0, V \rightarrow 0$

what happens between  $+ = 0$  and  $+ = \infty$ ?

$$I = -\frac{dQ}{dt} \quad \underline{\text{sign: }} Q \downarrow I \uparrow$$

$$= \frac{V}{R} = \frac{Q}{RC}$$

$$\frac{dQ}{Q} = -\frac{dt}{RC}$$

$$\ln Q = -\frac{t}{RC} + \text{constant}$$


$$Q = (\text{another Constant}) \cdot e^{-t/RC}$$


$$t=0, Q=Q_0$$

$$Q = Q_0 e^{-t/RC}$$

$$I = -\frac{dQ}{dt} = \frac{Q_0}{RC} e^{-t/RC} \quad (t \geq 0)$$
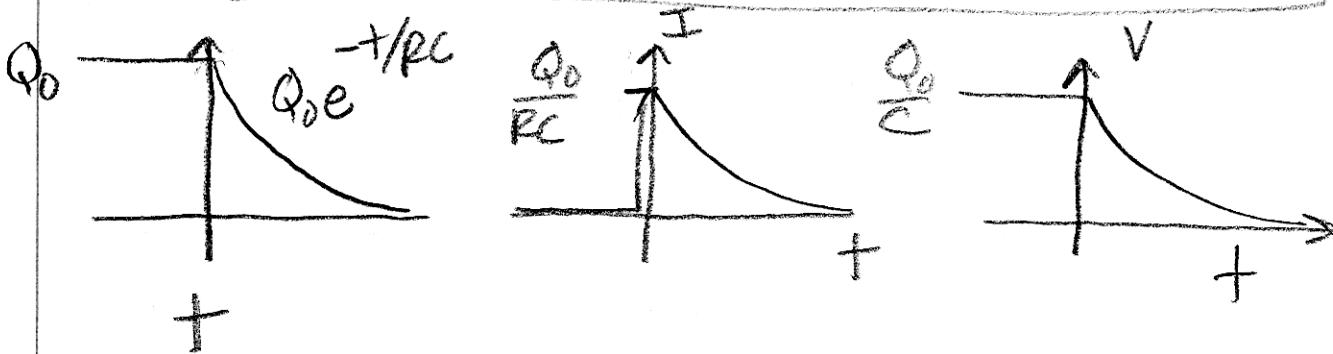
$$V = \frac{Q}{C} = RI = \frac{Q_0}{C} e^{-t/RC}$$



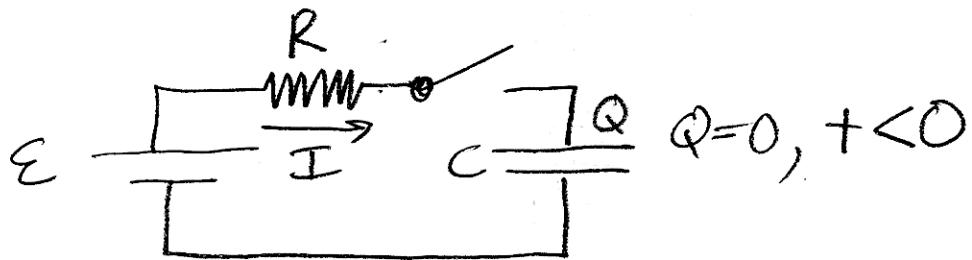

Close switch at  $+ = 0_-$  what happens?

$\rightarrow$  gradually C "charges up"; gets more voltage..

$\rightarrow + = 0$ : current across resistor will be.

$$I = \frac{\epsilon}{R}$$

$\rightarrow$  all time

now:  $\frac{dQ}{dt} = I$  (current charges,  
not discharges)

$$\epsilon - R \frac{dQ}{dt} - \frac{Q}{C} = 0$$

$$\frac{1}{C}(Q - C\epsilon) = -R \frac{dQ}{dt}$$

$$\tilde{Q} = Q - C\epsilon$$

$$\frac{d\tilde{Q}}{dt} = \frac{dQ}{dt}$$

so  $\frac{d\tilde{Q}}{dt} = -\frac{\tilde{Q}}{RC} \Rightarrow \tilde{Q} = \tilde{Q}_0 e^{-t/RC}$

$$Q = \hat{Q} + CE$$

$$Q = \hat{Q}_0 e^{-t/RC} + CE$$

$$Q(0) = 0 = \hat{Q}_0 + CE \Rightarrow CE = -\hat{Q}_0$$

$$Q = (1 - e^{-t/RC})CE$$

$$V = \frac{Q}{C} = (1 - e^{-t/RC})E$$

$$I = \frac{dQ}{dt} = \frac{E}{R} e^{-t/RC}$$

$+ > 0$

