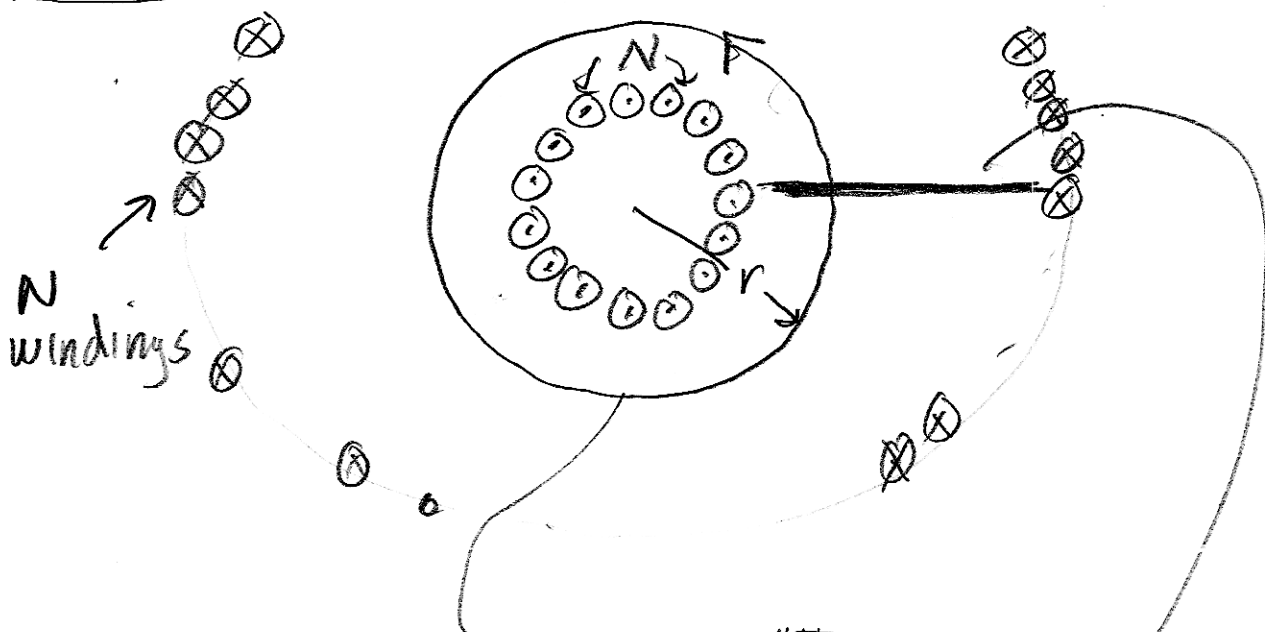



Cross sectional view:



$$2\pi r \cdot B = \frac{4\pi}{c} \cdot N \cdot I$$

$$B = \frac{2NI}{cr}$$

flux through this surface is

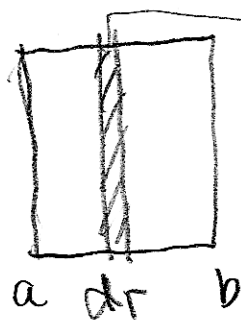

$$d\Phi_{BI} = \frac{2NI}{cr} \cdot h$$

$$\Phi_{BI} = \frac{2NIh}{c} \int_a^b \frac{dr}{r} = \frac{2NIh}{c} \ln\left(\frac{b}{a}\right)$$

There are N "loops" in the toroid.


$$\Phi_B = N \Phi_{BI} = \frac{2N^2 I h}{c} \ln\left(\frac{b}{a}\right)$$

$$\mathcal{E} = -\frac{1}{c} \frac{d\Phi_B}{dt} = -\frac{2N^2 h}{c^2} \ln\left(\frac{b}{a}\right) \frac{dI}{dt}$$

$$L = \frac{2N^2 h}{c^2} \ln\left(\frac{b}{a}\right) \quad \text{cgs}$$

$$L (\text{henrys}) = (2 \cdot 10^{-9}) N^2 h \ln\left(\frac{b}{a}\right)$$


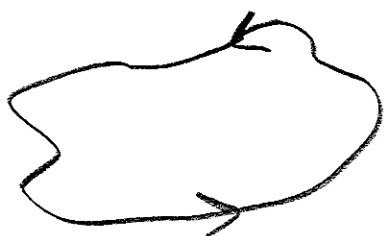
Turns out:
self inductance of a loop of
wire.



is hard to
compute!
(but not to measure).

Self inductance ... what inductors
have!

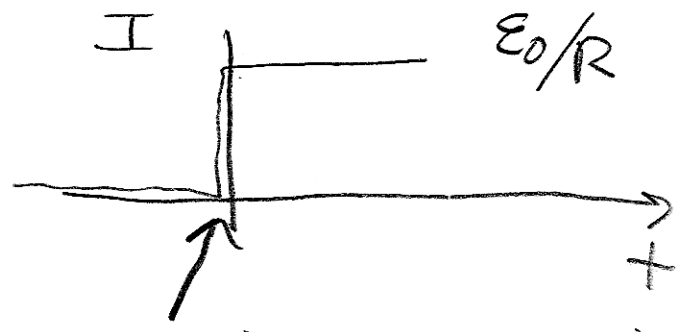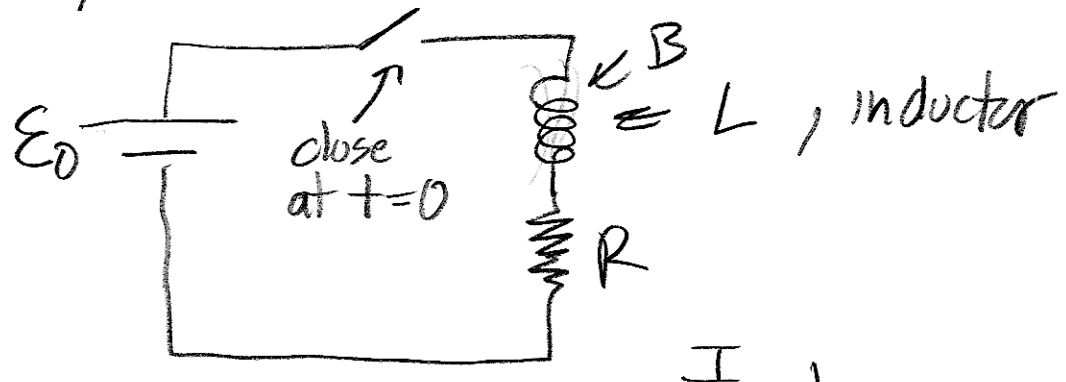$I \rightarrow \text{amps}$
 $h \rightarrow \text{cm!}$




No inductor ...

Inductor opposes the big change in current at $t=0$!

$$\mathcal{E}_0 - L \frac{dI}{dt} = RI$$

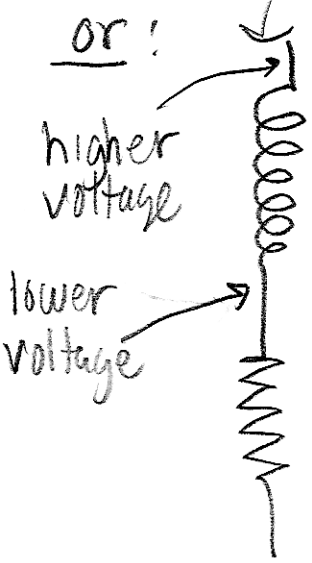↑ increase in I causes reduction in \mathcal{E}




\vec{E} field arrow is direction of increasing $\frac{dI}{dt}$

$$\mathcal{E}_0 = L \frac{dI}{dt} + RI$$

+ a little greater than 0... $\frac{dI}{dt}$ dominates...

$$\frac{dI}{dt} = \frac{\mathcal{E}_0}{L} \quad , \quad I \approx \frac{\mathcal{E}_0}{L} t$$
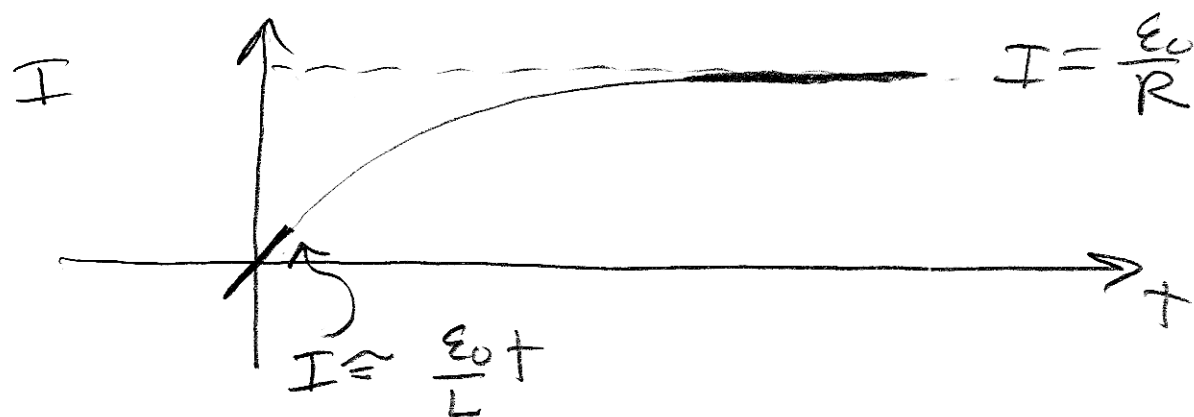
$$t \rightarrow \infty \quad \dots \quad I = \frac{\mathcal{E}_0}{R}$$



$$I = \frac{\mathcal{E}_0}{R} \left(1 - e^{-\left(\frac{R}{L}\right)t} \right)$$

vanishes as $t \rightarrow \infty$


when $t \sim 0$

$$e^{-\left(\frac{R}{L}\right)t} \approx 1 - \left(\frac{R}{L}\right)t + \dots$$

$$I \approx \frac{\mathcal{E}_0}{R} \left(1 - \left(1 - \left(\frac{R}{L}\right)t \right) \right) \approx \frac{\mathcal{E}_0}{R} \cdot \frac{R}{L} t$$


$$\approx \frac{\mathcal{E}_0}{L} t$$

visualization is!

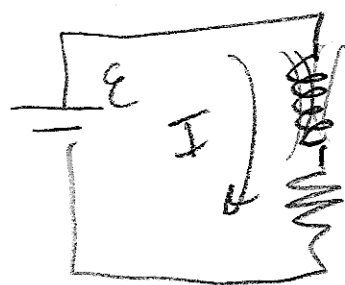

← takes a while to build up this energy

Suppose switch then opened.

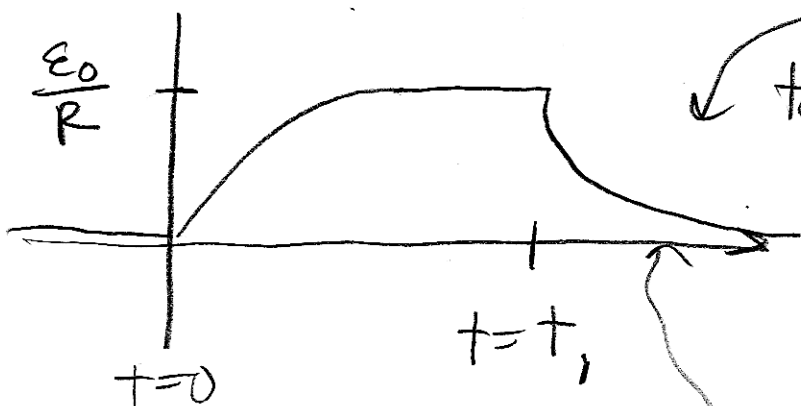

takes a while for the energy in the inductor to decay

$$I = \frac{\epsilon_0}{R} e^{-\frac{R}{L}(t-t_1)}$$

$$= I_0 e^{-\frac{R}{L}(t-t_1)}$$

How much energy?

$$U = \int_{t_1}^{\infty} I^2 R dt = I_0^2 R \int_{t_1}^{\infty} e^{-\frac{2R}{L}(t-t_1)} dt$$

↑
power

$x = \frac{2R}{L}(t-t_1)$

$$= I_0^2 R \int_0^{\infty} e^{-x} dx \times \frac{L}{2R}$$

$$U = \frac{1}{2} L I_0^2$$

can be thought of