

Physics 25 Problem Set 2

Harry Nelson

due Monday, April 17

Please make your work neat, clear, and easy to follow. It is hard to grade sloppy work accurately. Generally, make a clear diagram, and label quantities. Derive symbolic answers, and then plug in numbers after a symbolic answer is available.

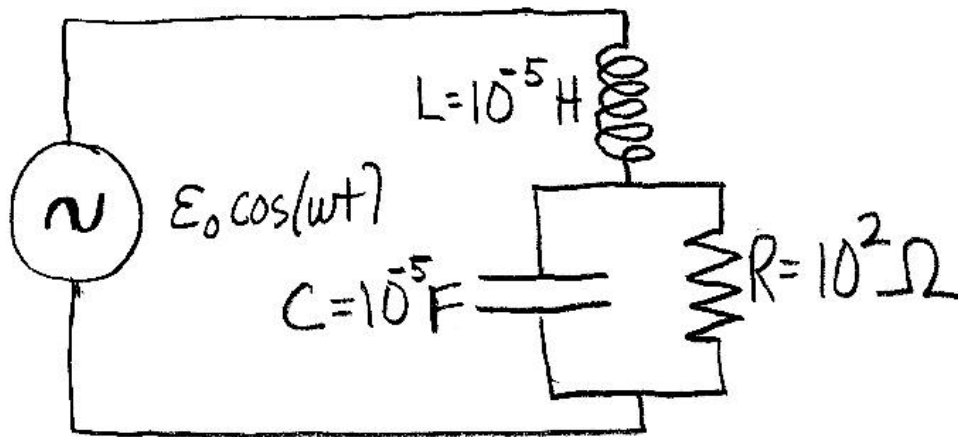


Figure 1: For use in Problem 1.

1. A power supply provides a sinusoidal voltage with $\epsilon_0 = 10$ V that is applied to the circuit shown in Fig. 1. The values of the passive components are $L = 10^{-5}$ H, $C = 10^{-5}$ F, and $R = 100$ Ω . The frequency ω is varied between $\omega_1 = 5 \times 10^4$ Hz and $\omega_2 = 2 \times 10^5$ Hz.
 - (a) Evaluate and plot the magnitude of the peak current flowing out of the power supply as a function of ω for ω between ω_1 and ω_2 , and use a logarithmic scale for the peak current. For what frequency ω_0 is the peak current a maximum?
 - (b) Evaluate and plot the phase between the current and the voltage for the same range of ω .
 - (c) Evaluate and plot the average power dissipated in the circuit for the same range of ω , and use a logarithmic scale for the power. How does the peak power dissipation compare with the very naive estimate of $\epsilon_0^2/(2R)$?
 - (d) Evaluate and plot the average power dissipated in the circuit for a very narrow range of ω , between $\omega_1 = 0.98 \times 10^5$ Hz and $\omega_2 = 1.02 \times 10^5$ Hz. Find the two frequencies where the power dissipation is one-half of the peak power; denote the difference between the two frequencies as $2\Delta\omega$, and evaluate $\omega_0/(2\Delta\omega)$, and compare this quantity to $R/(\omega_0 L)$.
 2. Purcell 9.2
 3. Purcell 9.5
 4. Purcell 9.9
 5. Purcell 9.10
-