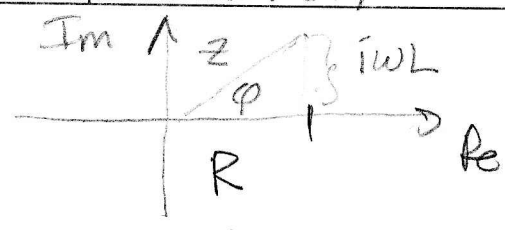


$$\frac{\epsilon_0}{R + i\omega L}$$



$$z = \sqrt{R^2 + (\omega L)^2} e^{i\phi} \quad \tan\phi = \frac{\omega L}{R}$$


$$I_0 = \frac{\epsilon_0}{\sqrt{R^2 + (\omega L)^2}} e^{-i\phi}$$

$$I = I_0 e^{i(\omega t - \phi)}$$

really, $\text{Re}[I] = \frac{\epsilon_0}{\sqrt{R^2 + (\omega L)^2}} \cos(\omega t - \phi)$

$$\phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

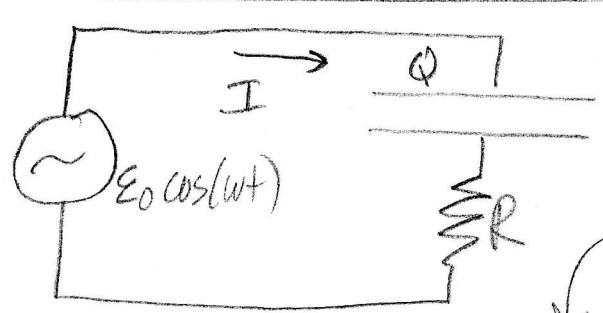+ : must "get over" ϕ ,
so shift of I is "forward"



← here, $\frac{dQ}{dt} = I$

$$\frac{Q}{C} + IR = \epsilon_0 \cos(\omega t)$$

try $I = I_0 e^{i\omega t}$
 $Q = \int I dt = \frac{I_0}{i\omega} e^{i\omega t}$

$$\left(\frac{I_0}{i\omega C} + I_0 R\right) e^{i\omega t} = \epsilon_0 e^{i\omega t}$$

$$I_0 = \frac{\epsilon_0}{R + \frac{i}{\omega C}} = \frac{\epsilon_0}{R - \frac{i}{\omega C}}$$

- sign.




$$\omega L \rightarrow -\frac{1}{\omega C}$$

$$\text{Re}[I] = \frac{\epsilon_0}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \cos(\omega t + \phi)$$

$$\phi = \tan^{-1}\left(\frac{1}{\omega RC}\right)$$

"small" effect: small inductor, small ω
 large capacitor, large ω

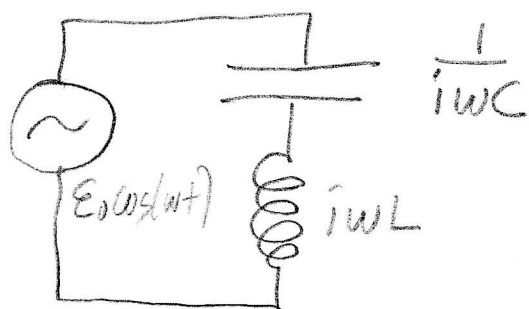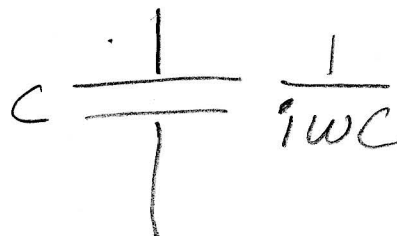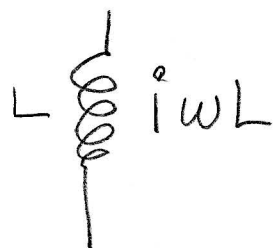The preceding can be summarized with the concept of impedance, "generalized" resistance.




$$I_0 = \frac{\epsilon_0}{\frac{1}{i\omega C} + i\omega L}$$

$$= i \frac{\epsilon_0}{\left(\omega L - \frac{1}{\omega C}\right)}$$

$$= \frac{\epsilon_0}{\omega L - \frac{1}{\omega C}} \cdot (-i = e^{-i\pi/2})$$
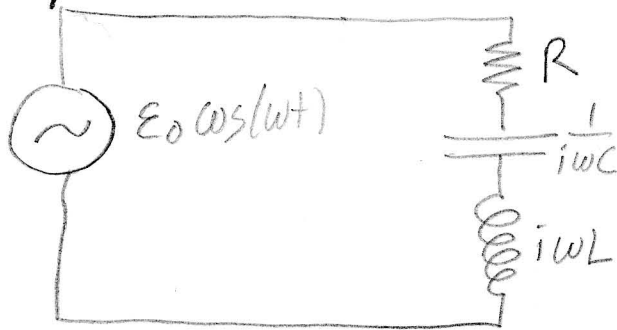
$$I = \frac{\epsilon_0}{\omega L - \frac{1}{\omega C}} \cos\left(\omega t - \frac{\pi}{2}\right) = \frac{\epsilon_0}{\omega L - \frac{1}{\omega C}} \sin(\omega t)$$



$$I_0 = \frac{\epsilon_0}{R + \frac{1}{i\omega C} + i\omega L} = \frac{\epsilon_0}{Z}$$

impedance

$$\equiv Y \cdot \epsilon_0$$

↑
admittance

$$\equiv \frac{1}{Z}$$

$$|I_0| = \frac{\epsilon_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$


$|I_0|$ maximum when $\omega L - \frac{1}{\omega C} = 0$


$$\omega^2 = \frac{1}{LC}$$

resonance at $\omega_0 = \frac{1}{\sqrt{LC}}$

at $\omega = \omega_0$ then $I_0 = \frac{\epsilon_0}{R}$ ← as though

"Resonant Circuit" ← 'smaller R

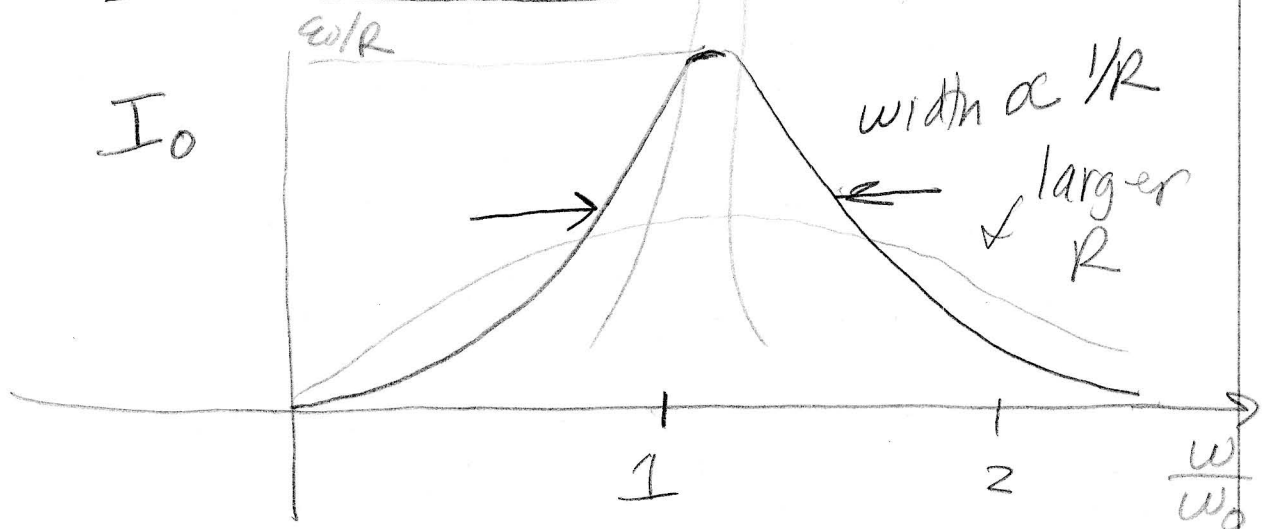

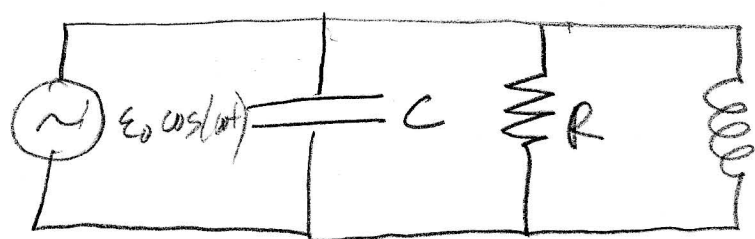

in parallel!

$$Y = \frac{1}{Z} = \left(\frac{1}{i\omega C}\right) + \frac{1}{R} + \frac{1}{i\omega L}$$

$$Y = \frac{1}{R} + i\omega C - \frac{i}{\omega L}$$

$$I_0 = Y \cdot \epsilon_0 = |Y| e^{i\phi}$$

$$|Y|^2 = \frac{1}{R^2} + \underbrace{\left(\omega C - \frac{1}{\omega L}\right)^2}$$


smallest now when

$$\omega_0 C - \frac{1}{\omega_0 L} = 0$$

$$\omega_0^2 = \frac{1}{LC} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

when $\omega = \omega_0$,

$$|Y| = \frac{1}{R}, \quad |I_0| = \frac{\epsilon_0}{R}$$

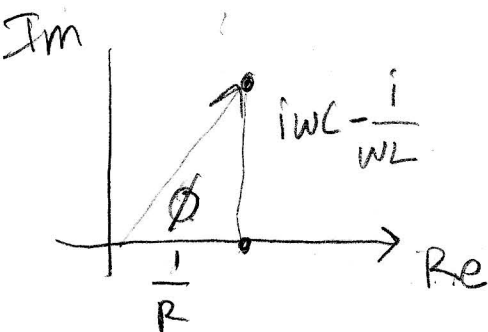
Phase: (look at admittance).

$$\phi = \tan^{-1} \left(\frac{\omega C - \frac{1}{\omega L}}{\frac{1}{R}} \right)$$

$$= \tan^{-1} \left(\omega R L - \frac{R}{\omega L} \right)$$

R=0?

Power ;

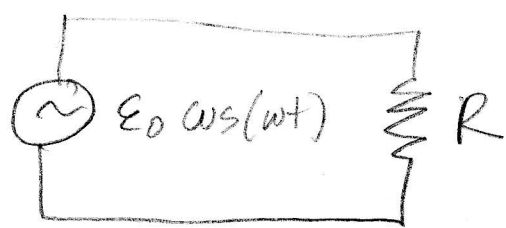


$$P = \frac{\epsilon_0^2}{R} \cos^2 \omega t$$

↑
instantaneous

$$\langle P \rangle = \frac{1}{2} \frac{\epsilon_0^2}{R} = \frac{V_{\text{rms}}^2}{R}$$
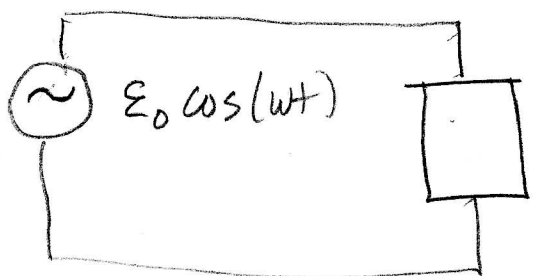
$$V_{\text{rms}}^2 = \frac{1}{2} \epsilon_0^2$$



$$Z = \frac{1}{Y}$$

$$Y = |Y| e^{i\phi}$$

$$I_0 = Y \epsilon_0 = |Y| e^{i\phi} \epsilon_0$$

instantaneous power : $P = I V$


$$\begin{aligned} &= \text{Re}[I] \cdot \text{Re}[V] \\ &= \text{Re}[I_0 e^{i\omega t}] \text{Re}[\epsilon_0 e^{i\omega t}] \\ &= \text{Re}[|Y| e^{i\phi} \epsilon_0 e^{i\omega t}] \text{Re}[\epsilon_0 e^{i\omega t}] \\ &= |Y| \epsilon_0^2 \underbrace{\cos(\omega t + \phi) \cos(\omega t)} \end{aligned}$$

$$\cos(\omega t) \cos \phi - \sin(\omega t) \sin \phi$$

$$\langle \cos^2(\omega t) \rangle = \frac{1}{2}$$

$$\langle \sin(\omega t) \cos(\omega t) \rangle = \langle \frac{1}{2} \sin(2\omega t) \rangle = 0$$


$$\langle P \rangle = \frac{1}{2} |Y| \epsilon_0^2 \cos \phi = \frac{I_{\text{rms}} V_{\text{rms}} \cos \phi}{\frac{1}{\sqrt{2}} |Y| \epsilon_0 \frac{1}{\sqrt{2}} \epsilon_0}$$

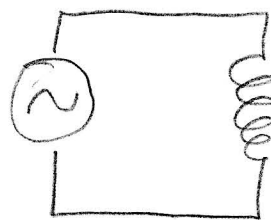 $i\omega L$

$$Y = \frac{1}{i\omega L} = \frac{-i}{\omega L} \quad \phi = -\frac{\pi}{2}$$

$$\cos(\phi) = 0!$$

no power
dissipated!

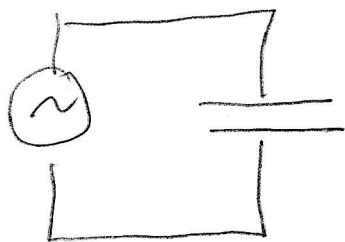 $\frac{1}{i\omega C}$

$$\cos(\phi) = 0$$

any combination of
L + C ... no power dissipation!
Need R ...